



Welcome to The Hardware Lab!

Fall 2018

Lab 5: Keyboard and Audio Modules

Prof. Chun-Yi Lee

Department of Computer Science
National Tsing Hua University

Agenda

- Lab 5 Outline
- Lab 5 Basic Questions
- Lab 5 Advanced Questions



Lab 5 Outline

- Basic questions (2%)
 - Individual assignment
 - Due on **11/15/2018**. Demonstration on your FPGA board (**In class**)
 - Only demonstration is necessary. Nothing to submit.
- Advanced questions (5%)
 - Group assignment
 - ILMS submission due on **11/22/2018. 23:59:59**.
 - Demonstration on your FPGA board (**In class**)
 - Assignment submission (**Submit to ILMS**)
 - Source codes and testbenches
 - Lab report in PDF

Lab 5 Rules

- You can use **ANY** modeling techniques
- If not specifically mentioned, we assume the following SPEC
 - **CLK** is **positive edge triggered**
 - Synchronously reset the Flip-Flops when **RESET == 1'b0**

Lab 5 Submission Requirements

- Source codes and testbenches
 - Please follow the templates **EXACTLY**
 - We will test your codes by TAs' testbenches
- Lab 5 report
 - Please submit your report in a single **PDF** file
 - Please **draw** the **block diagrams** and **state transition diagrams** of your designs
 - Please **explain** your designs in detail
 - Please **list** the contributions of each team member clearly
 - **Please explain how you test your design**
 - What you have **learned** from Lab 5

Agenda

- Lab 5 Outline
- **Lab 5 Basic Questions**
- Lab 5 Advanced Questions



Basic Questions

- Individual assignment
- FPGA demonstration (due on 11/15/2018. In class.)
 - Keyboard sample code
 - Audio sample code 1 & 2
 - Mixed keyboard and audio modules together
- Demonstrate your work by [waveforms](#)

Basic FPGA Demonstration 1

- **Keyboard sample code**



- Please implement the keyboard sample codes released on ILMS

- **Audio sample codes**

- Please implement the audio sample codes 1 & 2 released on ILMS

Basic FPGA Demonstration 2

- Use the numbers ("0" and "1") on the keyboard to control the scale to ascend or descend, ranging from **C4** to high **C8**.
- Change a note every **0.5 second**. If "2" is pressed, change a note every 1 second. If "2" is pressed again, go back to **0.5 second** per note.
- When it reaches **C4** or **C8**, stay on the note until the direction changes (keyboard pressed).

Button	Direction Reset: Set back to C4 and ascend (0.5sec/note) (Use Enter as Reset)
0	 <p>C4 D4 E4 F4 G4 A4 B4 C5 D5 E5 F5 G5 A5 B5 C6</p>
1	 <p>C4 D4 E4 F4 G4 A4 B4 C5 D5 E5 F5 G5 A5 B5 C6</p>
2	0.5 sec per note or 1 sec per note

Agenda

- Lab 5 Outline
- Lab 5 Basic Questions
- **Lab 5 Advanced Questions**




Advanced Questions

- Group assignment
- Verilog questions (due on 11/22/2018. 23:59:59.)
 - Mealy machine multi-sequence detector
 - Sliding window sequence detector
 - Traffic light controller
- FPGA demonstration (due on 11/22/2018. In class.)
 - Vending machine

Verilog Question 1


■ Mealy machine multi-sequence detector

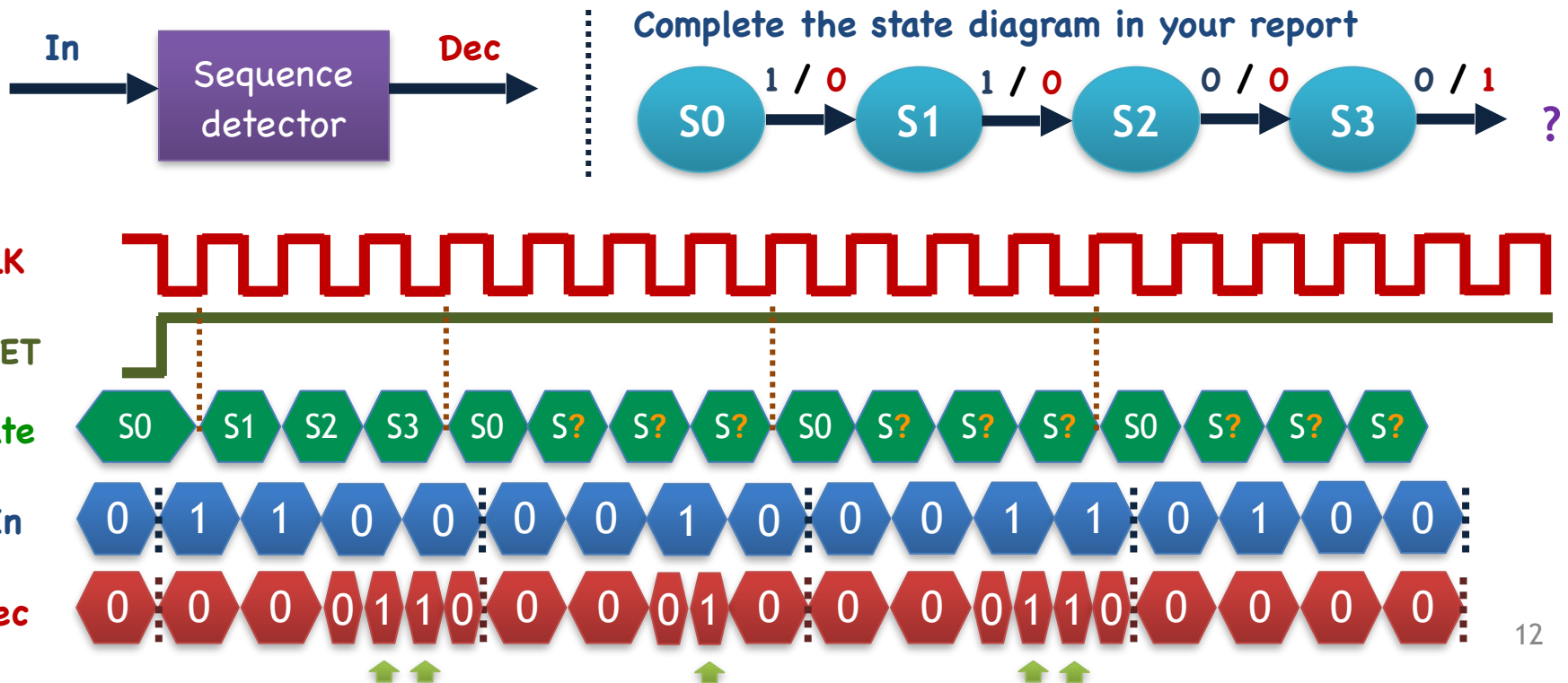- 1-bit input **In** and 1-bit output **Dec**
- When the four bit sequence is either **1100** or **0011**, **Dec** is set to **1**
- Re-detect the sequence **every four bits**
- Please draw your state diagram in your report




Verilog Question 2

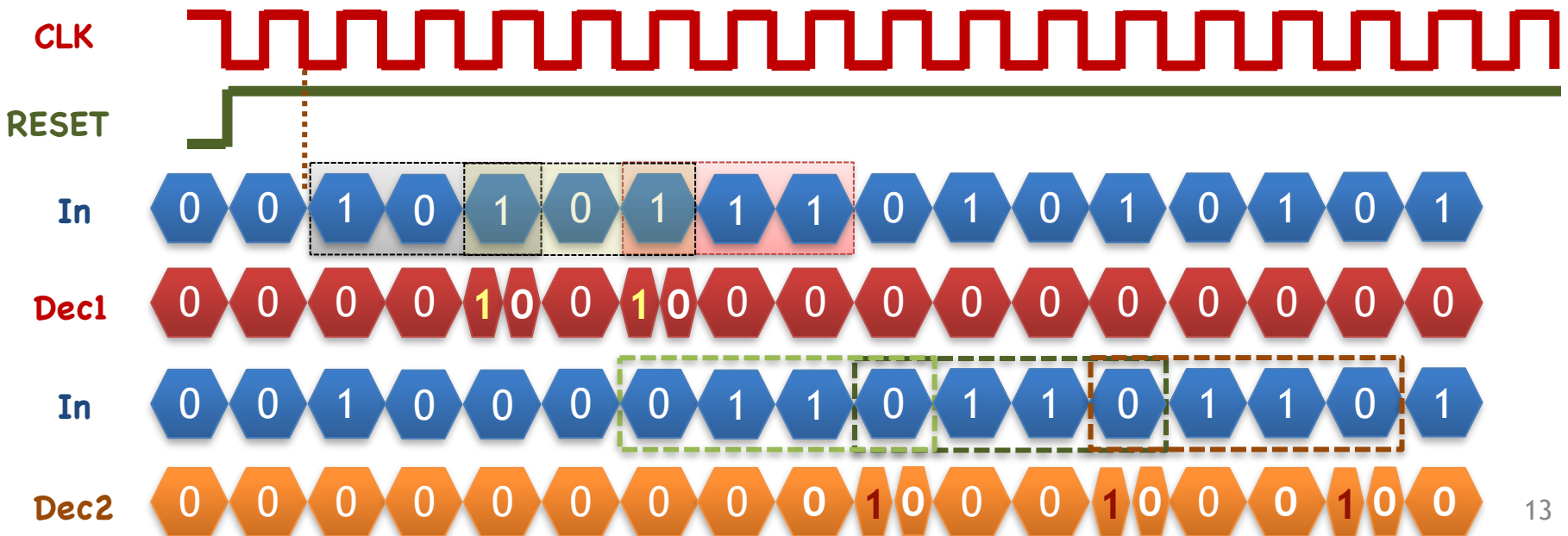- **Sliding Window** sequence detector (**mealy machine**)
 - Dec1 == 1'b1 when input is **101** AND no **111** occurs before
 - Dec2 == 1'b1 when input sequence is **0110**
- **Continuous detection**
 - Detect the sequences whenever they occur
 - Please draw a state transition diagram in your report




Verilog Question 3

- **Traffic light controller** for highway (HW) and local road (LR) intersection
- **HW** has higher priority and should be green as long as possible
- **LR** has a sensor to detect cars on it. When a car is sensed, LR turns green shortly
- Green light is **at least 25** clock cycles and yellow light is **5** clock cycles
- **Input:** **CLK**, **RESET**, LR_has_Car; **Output:** HW_light[2:0], LR_light[2:0]
- HW_light & LR_light: bits [2:0] represent **Red**, **Yellow**, and **Green**, respectively

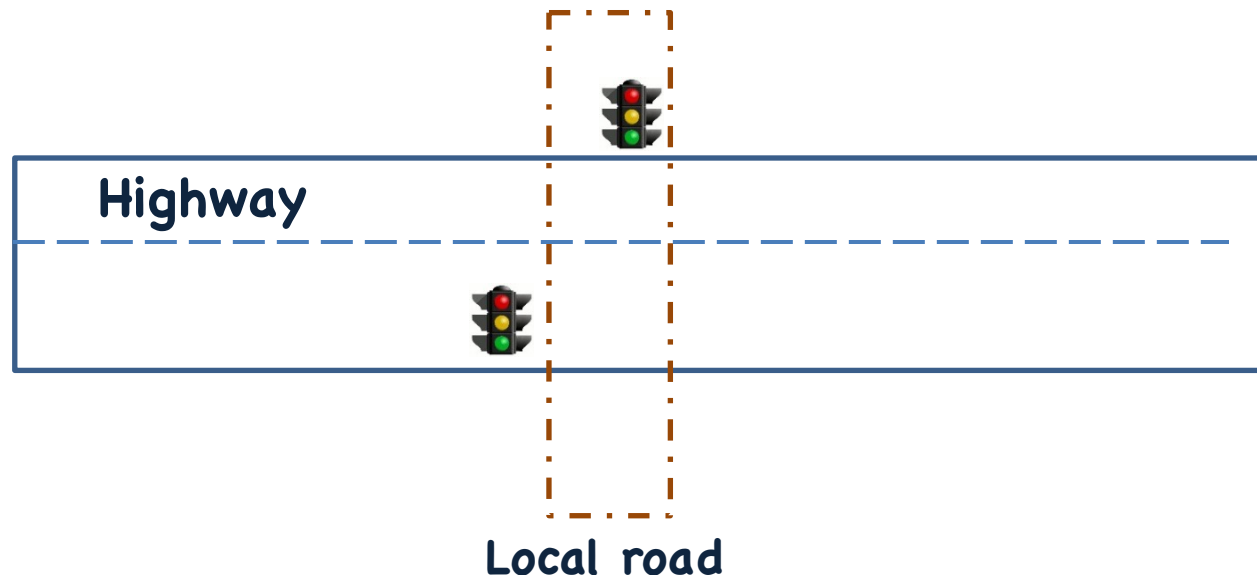


Verilog Question 3

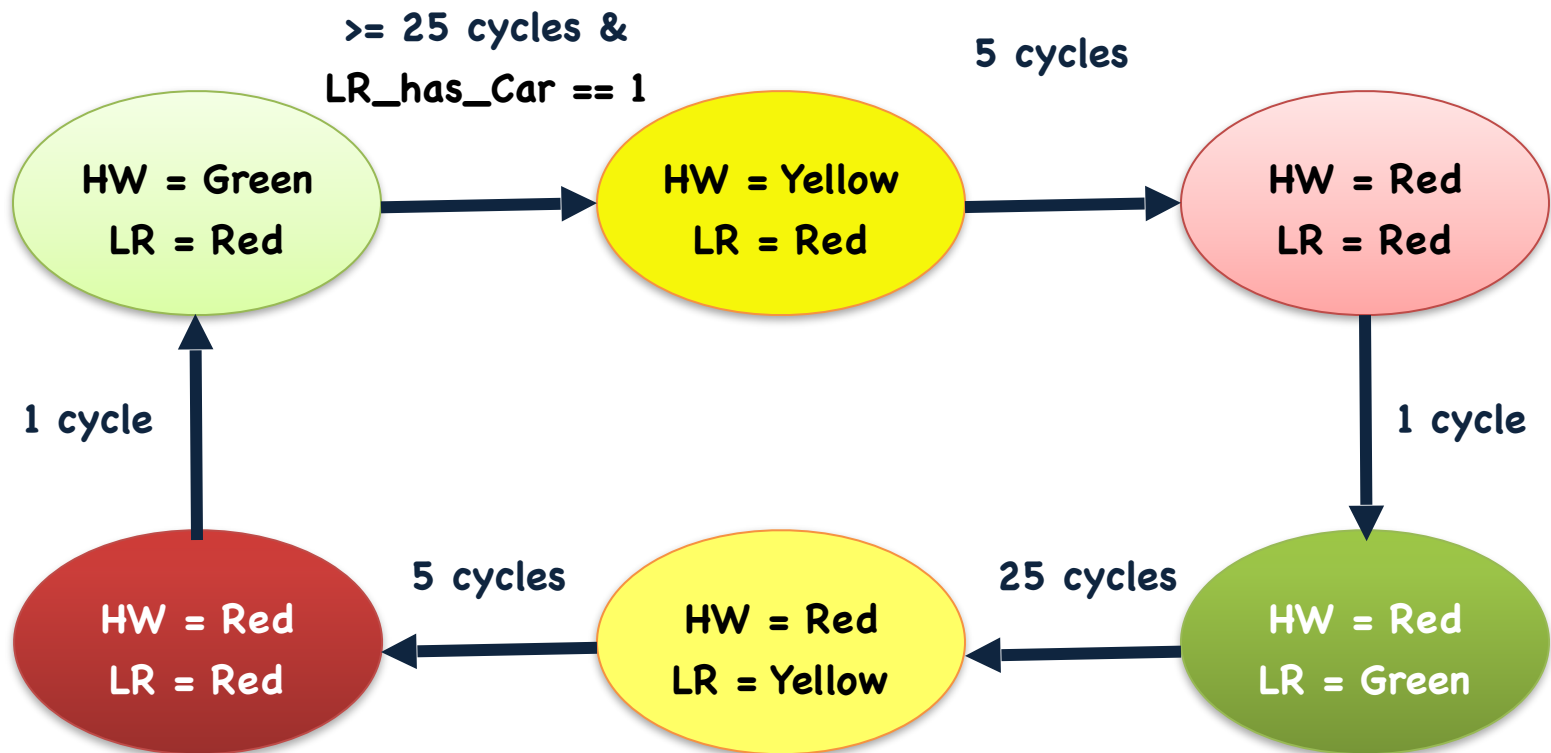- Traffic light controller Finite State Machine
- Please complete the FSM in your report (some arrows are removed intentionally)



Verilog Question 3

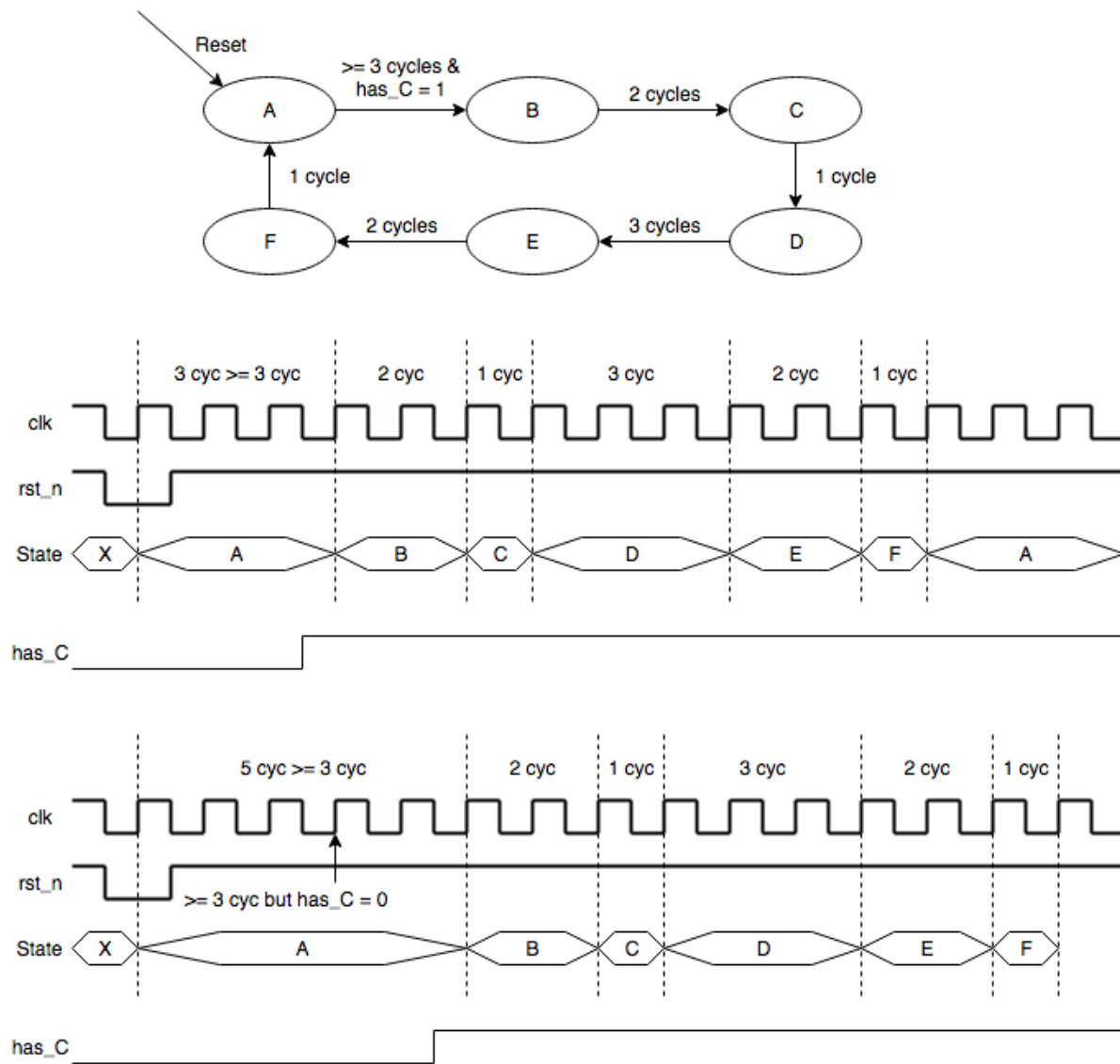

- Traffic light controller **"example"** timing diagram is illustrated on the left

- Please make sure that your state transitions follows the timing diagram correctly

Advanced Questions

- Group assignment
- Verilog questions (due on 11/22/2018. 23:59:59.)
 - Mealy machine multi-sequence detector
 - Sliding window sequence detector
 - Traffic light controller
- FPGA demonstration (due on 11/22/2018. In class.)
 - Stopwatch

FPGA Demonstration 1

- Four options available: **Coffee**, **Coke**, **Oolong**, and **Water**
- Prices are: **Coffee (NT\$ 55)**, **Coke (NT\$ 20)**, **Oolong (NT\$ 25)**, **Water (NT\$ 30)**
- The **rightmost two 7-segment displays** show the money inserted into the machine
 - When RESET == **1'b1**, please display "00"
 - The maximum value is **NT\$ 80**
- Use **five buttons** to implement your design:
 - Left: **NT\$ 5**
 - Center: **NT\$ 10**
 - Right: **NT\$ 50**
 - Top: **RESET**
 - Bottom: **Cancel**



FPGA Demonstration 1

- Use **four LEDs** to indicate which drinks you can buy
 - **LED[3:0]** corresponds to Coffee, Coke, Oolong, and Water, respectively
- Use the **keyboard** to select which drinks you can buy
 - **'a', 's', 'd', 'f'** corresponds to **Coffee**, **Coke**, **Oolong**, and **Water**, respectively
 - Assume that the machine allows you to buy **ONLY ONE DRINK** at a time
- Use the **rightmost two 7-segment display** to **show the rest of the money** after buying a drink
 - E.g., if you inserted **NT\$ 40** and bought a can of Coke (**NT\$ 20**), the 7-segment display will show **NT\$ 20**

FPGA Demonstration 1

- Remember to add debounce and one-pulse circuits to your buttons
- Decrement the **7-segment display** by **NT\$ 5** every second to mimic the process of returning changes
 - Return the changes until it becomes zero
- If the buyer does not want to buy a drink, he/she can use a **Cancel Button** to cancel it
 - The inserted money will be returned the same way (**NT\$ 5** per second)

The layout of the
buttons used in this
question



Insert
NT\$ 5



RESET



Insert
NT\$ 10



Insert
NT\$ 50



Cancel

Thank you for your attention!



*Lake Helen at Lassen Volcanic National Park, Shasta County, California, USA
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography